STELLA MARIS COLLEGE (AUTONOMOUS) CHENNAI – 600 086. (For candidates admitted during the academic year 2019 – 2020 and thereafter) SUBJECT CODE : 19PH/PC/EL14 M.Sc., DEGREE EXAMINATION NOVEMBER 2022

PHYSICS

FIRST SEMESTER

COURSE	:	MAJOR CORE
PAPER	:	ELECTRONICS - I
TIME	:	3 HOURS

MAX. MARKS : 100

(10x3=30)

SECTION - A

ANSWER ALL QUESTIONS:

1. What is transconductance? Mention its significance.

- 2. What is meant by pinch-off voltage in FET?
- 3. Differentiate between a counter and a register.
- 4. What is I^2L logic? Mention its advantages.
- 5. Mention few characteristics of op-amp.
- 6. What is a transducer? Mentions few of its applications.
- 7. How many interrupts does 8085 have? Mention them.
- 8. Differentiate between instruction cycle and machine cycle in 8085.
- 9. What are the basic operational modes of 8255?
- 10. Give the meaning of the control signals STB, IBF, INTR in 8255.

SECTION – B

ANSWER ANY FIVE QUESTIONS:

- 11. How is SCR used as half wave and full wave rectifier?
- 12. Give the characteristics of TRIAC.
- 13. Explain the working of Maser-Slave flip-flop.
- 14. Describe the working of up-down counter
- 15. Explain the working of 555 timer as monostable multivibrator.
- 16. Explain the various addressing modes in 8085.
- 17. Explain the interfacing of multiplexed 7 segment display using 8255.

SECTION – C

ANSWER ANY THREE QUESTIONS:

- 18. (a) Explain the FET characteristics with a neat graphs. (b) How is FET used as common drain amplifier?
- 19. (a) Differentiate between asynchronous and synchronous counters. (b) Explain the working of ripple counter. (c) Discuss the working of mod-8 counter
- 20. Design a circuit with op-amps to solve the following (a) simultaneous equations, x+y=3 and 2x+3y=7, (b) second order differential equation, $\frac{d^2x}{dt^2} + 4\frac{dx}{dt} + 25 =$

sin(20t + 36).

- 21. Explain with a neat diagrams, (a) the architecture of 8085, (b) the timing diagram for memory READ and memory WRITE cycles.
- 22. Discuss the interfacing (a) ADC and (b) Stepper motor with 8255.

(3x15=45)

(5x5=25)