

**STELLA MARIS COLLEGE (AUTONOMOUS) CHENNAI – 600 086.**  
**(For candidates admitted during the academic year 2011-12 & thereafter)**

**SUBJECT CODE: 11PH/MC/SE64**  
**B.Sc. DEGREE EXAMINATION APRIL 2017**  
**BRANCH III - PHYSICS**  
**SIXTH SEMESTER**

**REG. No.** \_\_\_\_\_

**COURSE : MAJOR – CORE**  
**PAPER : SEMICONDUCTOR ELECTRONICS**  
**TIME : 30 MINS. MAX. MARKS: 30**

**SECTION – A**

**TO BE ANSWERED ON THE QUESTION PAPER ITSELF**

**ANSWER ALL QUESTIONS: (30 x 1 = 30)**

**I Choose the Correct Answer:**

1. Transistors are made by \_\_\_\_\_  
a. superconductors      b. conductors      c. semiconductors      d. insulators
2. The emitter of transistor is always \_\_\_\_\_ biased with respect to base  
a. forward      b. reverse      c. emitter      d. base
3. The middle section of the transistor is \_\_\_\_\_  
a. emitter      b. gate      c. drain      d. base
4. In a transistor, the relation among the terms  $I_B$ ,  $I_C$  and  $I_E$  is  
a.  $I_C = I_E + I_B$       b.  $I_E = I_C + I_B$       c.  $I_E = I_C - I_B$       d.  $I_B = I_C + I_E$
5. The zero signal values of  $I_C$  and  $V_{CE}$  are known as the \_\_\_\_\_  
a. O point      b. I point      c. V point      d. Q point
6. The base of transistor is \_\_\_\_\_ doped  
a. lightly      b. moderately      c. highly      d. not
7. R.C. coupling is used to amplify \_\_\_\_\_  
a. current      b. sound      c. power      d. voltage
8. A JFET device acts like a \_\_\_\_\_  
a. diode      b. bipolar transistor      c. vacuum tube      d. triode
9. A JFET is characterized by \_\_\_\_\_ gain.  
a. power      b. voltage      c. current      d. source
10. Unit of transconductance is \_\_\_\_\_  
a. mho      b. ohm      c. ampere      d. volts
11. The device that exhibits negative resistance region is \_\_\_\_\_  
a. transistor      b. FET      c. UJT      d. opamp
12. The output pin number of opamp IC 741 is \_\_\_\_\_  
a. 7      b. 6      c. 5      d. 4

13. Find the value of  $CMRR_{dB}$  equivalent to  $CMRR$  value of 10.  
a. 200 dB                      b. 100 dB                      c. 20 dB                      d. 10 dB
14. Find the closed loop gain of non-inverting amplifier, if  $R_{in} = 1\text{ K}\Omega$  and  $R_f = 10\text{ K}\Omega$ .  
a. 11                              b. 10                              c. 9                              d. 0.1
15. \_\_\_\_\_ wave is an example of digital signal.  
a. Triangular                      b. Square                      c. Sinusoidal                      d. Saw tooth

**II Fill in the blanks:**

16. The function of transistor is \_\_\_\_\_.
17. A transistor circuit containing more than one stage of amplification is known as \_\_\_\_\_.
18. The bipolar transistor is a \_\_\_\_\_ controlled device.
19. The input impedance of opamp is \_\_\_\_\_.
20. The process of converting an analog voltage into digital signal is known as \_\_\_\_\_.

**III State whether true or false:**

21. An ideal value of stability factor is 0.
22. A transistor amplifier has high output impedance because collector has reverse biased.
23. A UJT has two pn junctions.
24. The operational amplifier is a versatile device.
25. A continuously varying signal is called an analog signal.

**IV Answer briefly:**

26. Define faithful amplification?
27. What is single stage transistor amplifier?
28. What is JFET?
29. Define differential amplifier.
30. What is digital to analog converter?



**STELLA MARIS COLLEGE (AUTONOMOUS) CHENNAI – 600 086.**  
**(For candidates admitted during the academic year 2011-12 & thereafter)**

**SUBJECT CODE: 11PH/MC/SE64**

**B.Sc. DEGREE EXAMINATION APRIL 2017**  
**BRANCH III - PHYSICS**  
**SIXTH SEMESTER**

**COURSE : MAJOR – CORE**  
**PAPER : SEMICONDUCTOR ELECTRONICS**  
**TIME : 2 ½ HOURS** **MAX. MARKS: 70**

**SECTION – B**

**ANSWER ANY FIVE QUESTIONS:**

**(5 x 5 = 25)**

1. Describe base resistor method for transistor biasing.
2. Draw the circuit of a practical single stage transistor amplifier. Explain the function of each component.
3. When  $V_{GS}$  of a JFET changes from -3.1V to -3.0V, the drain current changes from 1 mA to 1.3 mA. What is the value of transconductance?
4. Find the intrinsic stand off ratio for a UJT. Given that  $R_{B1} = 3 \text{ K}\Omega$  and  $R_{B2} = 2 \text{ K}\Omega$ .
5. A differential amplifier has an open circuit voltage gain of 100. The input signals are 3.25V and 3.15V. Determine the output voltage.
6. You have the following resistor values available: 1  $\text{K}\Omega$ , 5  $\text{K}\Omega$ , 10  $\text{K}\Omega$  and 20  $\text{K}\Omega$ . Design the opamp circuit to have a voltage gain of -4.
7. Explain digital to analog converter by using R-2R ladder method.

**SECTION – C**

**ANSWER ANY THREE QUESTIONS:**

**(3 X 15 = 45)**

8. Describe the voltage divider biasing method in detail?
9. Explain transistor RC coupled amplifier with special reference to frequency response.
10. Explain the construction and working of a UJT.
11. Discuss the following operation of an Opamp  
(i) subtractor (ii) differentiator and (iii) voltage follower
12. Explain analog to digital converter by using counter method.

▲▲▲▲▲▲▲▲▲▲